

5. a) What is op-Amp? Explain the various parameters of Operational Amplifier. [07 Marks] CO3 L2
- b) Sketch the circuits of each of the following based on the use of Op-amp along with input and output waveforms: [07 Marks] CO3 L2
i) Integrator ii) Voltage follower iii) Comparator
- c) List the characteristics of Operational Amplifier. [06 Marks] CO3 L2
- OR**
6. a) With neat circuit diagram explain inverting and non inverting Amplifier. [08 Marks] CO3 L2
- b) With neat circuit diagram explain the summing Amplifier and Differential Amplifier. [08 Marks] CO3 L2
- c) An inverting op-amp is to operate according to the following specifications, Voltage gain=100, Input resistance=10k, Lower cutoff frequency=250Hz, upper cutoff frequency=15kHz, Design the circuit to satisfy the above specification using an Operational Amplifier. [04 Marks] CO3 L2
7. a) Convert a) $(AC12)_{16} = (?)_8 = (?)_2$ [08 Marks] CO4 L2
b) $(3276.3607)_8 = (?)_2 = (?)_{16}$.
- b) State and prove De Morgan's theorem for two variables. [06 Marks] CO4 L2
- c) Write the typical schematic arrangement of microprocessor and Explain. [06 Marks] CO4 L2
- OR**
8. a) Explain different addressing modes of microprocessor with an example [08 Marks] CO4 L2
- b) Draw the symbol, truth table and expression for output for (i) NOT gate (ii) AND gate (iii) OR gate [06 Marks] CO4 L2
- c) Describe the working of the full adder using basic gates. [06 Marks] CO4 L2
9. a) Explain the schematic block diagram of basic communication system in detail. [08 Marks] CO5 L2
- b) What is noise? Explain the types of external noise. [06 Marks] CO5 L2
- c) Define the following. [06 Marks] CO5 L2
A.) Critical Frequency B.) Skip Distance C.) MUF D.) Fading
- OR**
10. a) Explain [10 Marks] CO5 L2
1.) Handoff management
2.) Location management
- b) With neat block diagram explain GSM architecture in detail. [10 Marks] CO5 L2